Project Components (Short Notes)

- 1. ATtiny85 / Arduino A microcontroller used to control all operations.
- 2. **TMP36 Temperature Sensor** Senses ambient temperature and outputs analog voltage.
- 3. **LEDs (Red, Green, Blue, White, etc.)** Visually indicate temperature range by blinking.
- 4. 220 Ohm Resistors Used to limit current to LEDs.
- 5. Coin Cell Battery (3V) Power supply for the project.
- 6. **DPST Switch** Used to turn the circuit ON/OFF.
- 7. Wires & Breadboard For making all connections.

Short Description of the Project

This project demonstrates the **interfacing of a TMP36 temperature sensor with an ATtiny85 (or Arduino)**. Depending on the **temperature readings**, different **LEDs blink** to indicate the current temperature range.

The analog voltage output from TMP36 is read by the microcontroller and converted into temperature using a formula. Based on the value, a specific LED color is turned ON or blinked. For example:

Below 10°C: Blue LED

10°C–15°C: Green LED

15°C–20°C: Yellow LED

Above 20°C: White or Red LED