

Circuit Connections:

1. LED Connections:

- Connect the **anode (longer leg)** of the LED to **digital pin 9** via a **220-ohm resistor**.
- Connect the **cathode (shorter leg)** to **GND**.

2. Potentiometer Connections:

- One outer pin to **5V**.
- Other outer pin to **GND**.
- Middle pin (wiper) to **analog pin A0**.

3. Power Source (optional for battery mode):

- Connect a 9V battery to the VIN and GND pins for mobile operation.
-

Working Principle:

- The potentiometer controls the analog input.
- The Arduino reads the analog value from **A0** (ranges from 0 to 1023).
- It maps this value to **PWM output** (0–255) to control **LED brightness**.
- More resistance = lower voltage = dimmer LED.
- Less resistance = higher voltage = brighter LED.